

《数字 VLSI》第二次作业


2022310976 江之行

$$1. F = \bar{A} + \bar{B}\bar{C} + \bar{D}$$

$$\bar{F} = \overline{\bar{A} + \bar{B}\bar{C} + \bar{D}}$$

$$= \bar{A} \cdot \bar{B}\bar{C} \cdot \bar{D}$$

$$= A \cdot (B+C) \cdot D$$

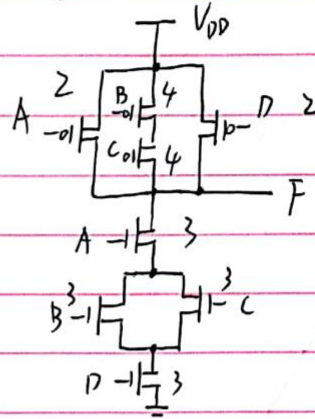

2. (1) 上升传播延时 t_{PLH} , 此时上管导通, 下管截止

① 初: $V_{G1} = V_{GS} - V_{TH} = 2.07V$, $V_{DS} = V_{DD} - 0 = 0.5V$, $V_{DSAT} = 0.63V$

$$\therefore I = k' \cdot \frac{W}{L} (V_{G1} \cdot V_{DS} - \frac{1}{2} V_{DS}^2) = 418.6 \mu A$$

$$R_1 = V_{DS} / I = 1.194 k\Omega$$

② 末: $V_{G1} = V_{GS} - V_{TH} = 1.82V$, $V_{DS} = V_{DD} - \frac{1}{2} V_{DD} = 0.25V$, $V_{DSAT} = 0.63V$

$$\therefore I = k' \cdot \frac{W}{L} (V_{G1} \cdot V_{DS} - \frac{1}{2} V_{DS}^2) = 194.9 \mu A$$

$$R_2 = V_{DS} / I = 1.283 k\Omega$$

③ $R_{eq1} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} + t_{PLH} = 0.69(R_1 + R_2) / 2 \cdot C = 855 ps$

(2) 下降传播延时 t_{PHL} , 此时下管导通, 上管截止

① 初: $V_{G1} = V_{GS} - V_{TH} = 2.07V$, $V_{DS} = 0.5V$, $V_{DSAT} = 0.63V$

$$\therefore I = k' \cdot \frac{W}{L} (V_{G1} \cdot V_{DS} - \frac{1}{2} V_{DS}^2) = 418.6 \mu A$$

$$R_1 = V_{DS} / I = 1.194 k\Omega$$

② 末: $V_{G1} = V_{GS} - V_{TH} = 2.07V$, $V_{DS} = 0.25V$, $V_{DSAT} = 0.63V$

$$\therefore I = k' \cdot \frac{W}{L} (V_{G1} \cdot V_{DS} - \frac{1}{2} V_{DS}^2) = 223.675 \mu A$$

$$R_2 = V_{DS} / I = 1.118 k\Omega$$

③ $t_{PHL} = 0.69(R_1 + R_2) / 2 \cdot C = 798 ps$ 年 月 日 第 页

3. $t = 0.69 [C_1 R_5 + C_2 R_5 + C_3 R_5 + C_4 R_5 + C_5 \cdot 0 + C_6 (R_5 + R_6) + C_7 R_5 + C_8 R_5 + C_9 (R_5 + R_6 + R_7)] = 759 ps$